

[Full Marks - 60

- [illegible]

- Q.2 a) Convert the following number to decimal. 6
 i) $(1101.11)_2$ ii) $(2F.A)_{16}$
 b) Perform following subtraction using one's and two's complement method. 5
 i) $(11101)_2 - (10010)_2$

OR

- Q.3 a) Convert following decimal no. to an equivalent binary number. 6
 i) $(16)_{10}$ ii) $(45)_{10}$ iii) $(25)_{10}$
 b) Solve the following. 5
 i) $(101110 + 011011)$ ii) $(1100 - 0110)$

- Q.4 a) Explain OR, AND and NOT gates with logic symbol and truth table. 5
 b) Prove associative and commutative laws of Boolean algebra with the help of truth table. 6

OR

- Q.5 a) Prove that, 4
 i) $A + BC = (A + B) \cdot (A + C)$
 ii) $A + \bar{A} \cdot B = A + B$
 b) Write any four duality theorems in boolean algebra. 2
 c) Explain NAND and NOR gate with logic symbol, truth table and logic equation. 5
 Q.6 a) Draw 2 variable, 3 variable and four variable K-map. 5
 b) What are Pair, Quad and Octet in K-map ? Explain with example. 6

OR

- Q.7 a) Convert following SOP equation into standard SOP equation. 4
 i) $Y = A\bar{B} + BC + A\bar{C}$
 ii) $Z = \bar{X}Y + \bar{W} \cdot \bar{Y} + X \cdot Z$
 b) What is K-map ? 2
 c) Minimize the following function using K-map and realize it using NAND gates only. 5
 $f(A,B,C,D) = \sum m(0,2,4,6,8,9,10,11,12,14)$
 Q.8 a) Construct and explain full adder circuit with two half adder circuit. 5
 b) What is Multiplexer ? Explain 4:1 multiplexer with logic diagram and truth table. 6

OR

- Q.9 a) Explain Half subtractor with logic diagram and truth-table. 4
 b) What is Encoder ? 2
 c) What is Demultiplexer ? Explain 1:4 demultiplexer with logic diagram and truth table. 5
 Q.10 a) Draw the logic diagram of clocked RS Flip-Flop and explain its working Truth- Table. 5
 b) Explain decade counter with logic diagram and Truth-Table and timing diagram. 6

OR