

OR

- Q.11 a) What are draw backs of RS FF? Explain JK FF 4
b) Draw and explain decade counter 5
c) What is T FF? Explain. 2

SCD - 4643

First Year B.C.A. (Semester - I) Examination

Paper - 15BCA103

Digital Techniques

Time: Three hours]

[Full Marks - 60

- N.B. :**
- i) All questions carry equal marks
 - ii) Due credit will be given to neatness & adequate dimensions.
 - iii) Assume suitable data wherever necessary.
 - iv) Diagrams & Equations should be given wherever necessary.
 - v) Use Blue/Black ink/refill only for writing the answer book.

Q.1 Select the correct alternative & rewrite the sentence 5

- a) Radix of binary number system is _____
i) 2 ii) 4
iii) 8 iv) 16
- b) _____ is the universal gate
i) NAND ii) Ex-OR
iii) NOT iv) OR
- c) 4-variable K-map has _____ squares for output.
i) 2 ii) 8
iii) 16 iv) 32
- d) 8 : 1 Mux has _____ select/control lines.
i) 1 ii) 2
iii) 3 iv) 4
- e) Modules of a decade counter is _____
i) 2 ii) 5
iii) 10 iv) 16

- Q.2 a) Find the value of x. 5
 i) $(100.75)_{10} = x_2$
 ii) $(1067.25)_8 = x_2$
 iii) $(AAA.A)_{16} = x_2$
 iv) $(11101.101)_2 = x_{10}$
 v) $(101111011.111)_2 = x_8$
 b) Perform following subtraction by using 1's complement method. 4
 i) $(1101)_2 - (1001)_2$
 ii) $(11101)_2 - (10111)_2$
 c) What are various types of number systems? Explain. 2

OR

- Q.3 a) Explain subtraction by 2's complement method with example. 4
 b) Explain conversion of decimal number to binary number. Give suitable example. 4
 c) What is BCD code? List its advantages. 3

- Q.4 a) NOR and NAND gates are called as universal gates. Explain. 4
 b) Explain various boolean laws. 4
 c) Prove following identity. 3
 i) $A + \overline{A}B = A + B$
 ii) $A \oplus B = AB + \overline{A}\overline{B}$

OR

- Q.5 a) State and prove DeMorgan's theorem. State gate equivalence of DeMorgan's theorems. 5
 b) Write short note on Ex-OR gate. 3
 c) What are different basic gates? Explain with truth table, logic equation, logic symbol and logical statement. 3

- Q.6 a) Explain pairs, quads and octet with respect to K-map. 3
 b) Draw 2, 3 and 4 variable K-map. 3
 c) Convert following equations into standard SOP form. 5
 i) $Y = AB + \overline{B}C + A\overline{C} + A$
 ii) $Y = ABC + A\overline{B}D + \overline{B}CD + \overline{A}CD$

OR

- Q.7 a) Explain the concept of SOP and POS with suitable example. 5
 b) Minimize the following functions using K-map and realise using universal gates. 6
 i) $f(A,B,C,D) = \sum m(0, 2, 3, 6, 7, 10, 11, 14, 15)$
 ii) $f(A,B,C,D) = \sum m(1, 3, 5, 7, 10, 14, 15)$

- Q.8 a) What is Full Adder? Explain the construction and working of full adder with neat diagram. 4
 b) What is encoder? Draw and explain Decimal to BCD encoder. 4
 c) What is Multiplexer? Explain 4 : 1 multiplexer. 3

OR

- Q.9 a) Draw & explain 4 BIT parallel Adder/subtractor. 4
 b) What is demultiplexer? Explain 1 : 4 demultiplexer. 4
 c) What is Half Adder? Explain. 3

- Q.10 a) Draw and Explain clocked RS FF using NOR gates. 4
 b) With neat block diagram explain 4 - BIT ripple counter. Also draw timing diagrams. 5
 c) What is Counter? What is modulus of a counter? Explain with example. 2